

**Electricity Study Guide**

- I. Charge in the atom
  - a. Atoms have protons (+), electrons (-) and neutrons (no charge)
  - b. Electricity is the flow of electrons...Electrons can move!

When charged particles come together, they exert a force.  
 The **electrical force** is a universal force that exists between any two charged objects.

- c. Opposite charges attract, similar charges repel




- d. Electrical energy can produce heat, light, motion, and sound

- II. Static electricity
  - a. Caused by a build-up of electrons (negative charge)
  - b. Electrons are discharged when they leave the site of the buildup (ex. Jump from your hand to the doorknob)
  - c. Rub a balloon on your hair and it builds up electrons. Place negatively charged balloon near the wall and it sticks.

- III. Current electricity
  - a. Flows through a path (circuit)
  - b. Direct current- flows in one direction (ex. batteries) from the negative end of the battery to the positive end.
  - c. Alternating current- generated at a power station (ex. electricity in the wall outlets)

- IV. Circuits
  - a. A circuit is a closed path through which electricity flow:


- b. A simple circuit has 3 parts

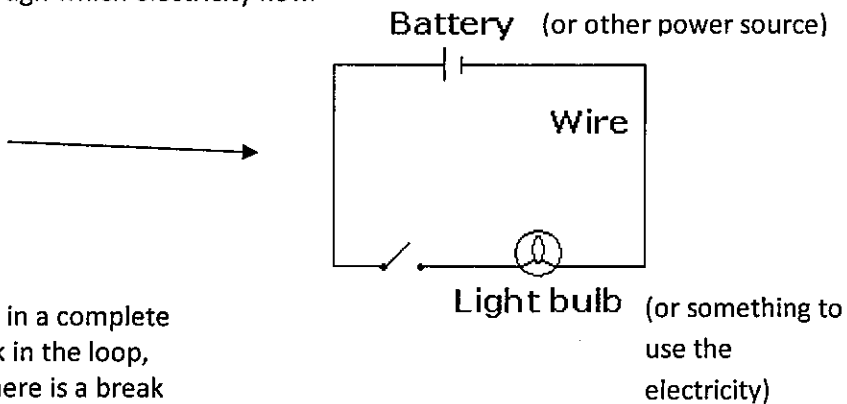

- c. An electrical circuit must run in a complete **loop**. When there is no break in the loop, it is a **closed circuit**. When there is a break in the loop, it is an **open circuit**. Electricity will **not flow** in an open circuit.

***Flip on the switch....close the circuit!!!***

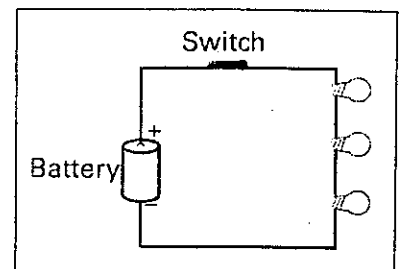
- V. Series Circuits
  - a. Series Circuit- all parts of the circuit are connected in a single loop.
  - b. An advantage of series circuits is that they are simpler.
  - c. 2 disadvantages:



- i. A break anywhere in the path stops the electron flow in the entire circuit. So...if one light bulb burns out, then they all burn out!
- ii. As more devices (e.g. light bulbs) are added to the circuit, the total resistance increases. This makes the circuit less efficient.

#### VI. Parallel Circuits

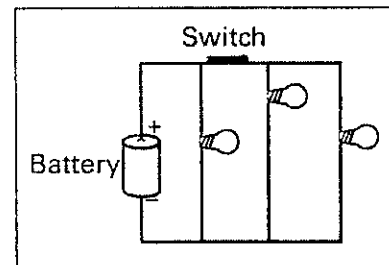- a. Have more than one path for the electricity to flow to each device.
- b. If one device (such as a light bulb) burns out, then the rest stay lit up!



#### VII. Electricity and Ohm's law

Electrons will flow from an area of high concentration (high potential energy) to an area of low concentration (low potential energy), but it takes **energy** to move the electrons

- a. **Ohm's law** shows the relationship between the voltage, current, and resistance.
- b. **Voltage (volts)**
  - a measure of the energy available to move electrons
  - the greater the voltage, the more electrons that may be moved
- c. **Current (amps)**
  - the flow of electrons through a wire
  - measured by counting the number of electrons that pass a given point each second
  - the greater the current, the greater the flow of electrons
- d. **Resistance**
  - the opposition to the flow of electrons
  - often produces heat, light, or mechanical energy as a result
  - the longer or thinner the wire or the greater the temperature, the greater the resistance

#### e. Ohm's Law formula:

$$I = V/R \quad \text{or} \quad \text{current} = \text{voltage} / \text{resistance}$$

#### VIII. Magnetism

- a. Natural magnets are found in cobalt, nickel, iron
- b. Magnets always have two poles: North and South
- c. Magnets can attract or repel each other (opposite poles attract, similar poles repel)
- d. Wrapping a nail with copper wire attached to a source of electricity (battery) can produce a magnet
- e. Moving a magnet in and out of a coil of wire will produce an electric current (like in a generator)